



UNIVERSITY OF
CAMBRIDGE
Department of Engineering

IB Paper 5 Electromagnetic Fields & Waves

Lecture 2 Transmission Lines II

<https://www.vle.cam.ac.uk/course/view.php?id=70081>

Characteristic Impedance

FLE99, GER86

- A transmission line consists of two or more conductors that guide the flow of energy in the form of an electromagnetic wave
- We looked at an equivalent circuit for a short length of an ideal transmission line to give the ***Telegrapher's Equations***

$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t} \qquad \frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t} \qquad (1.1)$$

- Combining these produced a ***wave equation*** for both current and voltage on the line

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2} \qquad \frac{\partial^2 I}{\partial x^2} = LC \frac{\partial^2 I}{\partial t^2} \qquad (1.3)$$

- The solution to these are equations for voltage and current as a function of position and time

$$V = \overline{V}_F e^{j(\omega t - \beta x)} + \overline{V}_B e^{j(\omega t + \beta x)} \qquad (1.11)$$

$$I = \overline{I}_F e^{j(\omega t - \beta x)} + \overline{I}_B e^{j(\omega t + \beta x)} \qquad (1.13)$$

- $\overline{V}_F, \overline{V}_B, \overline{I}_F$ and \overline{I}_B are complex numbers representing both the amplitude and phase offset of the voltage and current waves travelling in the positive x -direction (forward) and negative x -direction (backwards)
- An attenuation term is added to Eqns. 1.11 and 1.13 if the transmission line is 'lossy'

- The voltage and current on the transmission line are clearly related to each other by the Telegraphers Equations (Eqn. 1.1)


$$\frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t}$$

$$(-\beta \bar{I}_F e^{-j\beta x} + \beta \bar{I}_B e^{j\beta x}) = -C(\omega \bar{V}_F e^{-j\beta x} + \omega \bar{V}_B e^{j\beta x})$$

- We have cancelled the common factor of $j e^{j\omega t}$
- We can also separately equate the forward ($e^{-j\beta x}$) and backward ($e^{j\beta x}$) terms separately to give

$$\frac{\bar{V}_F}{\bar{I}_F} = \frac{\beta}{\omega C} \qquad \frac{\bar{V}_B}{-\bar{I}_B} = \frac{\beta}{\omega C} \qquad (2.1)$$

- Why are the equations for the relationship between V and I the same for both the forward and backward waves apart from the ‘-’ on \bar{I}_B ?
- The voltages are defined as being the voltage on the ‘upper’ conductor with respect to the lower, and the currents are defined as being in the positive x -direction
- When the wave is travelling in the negative x -direction, the current will be negative, but the voltage is not

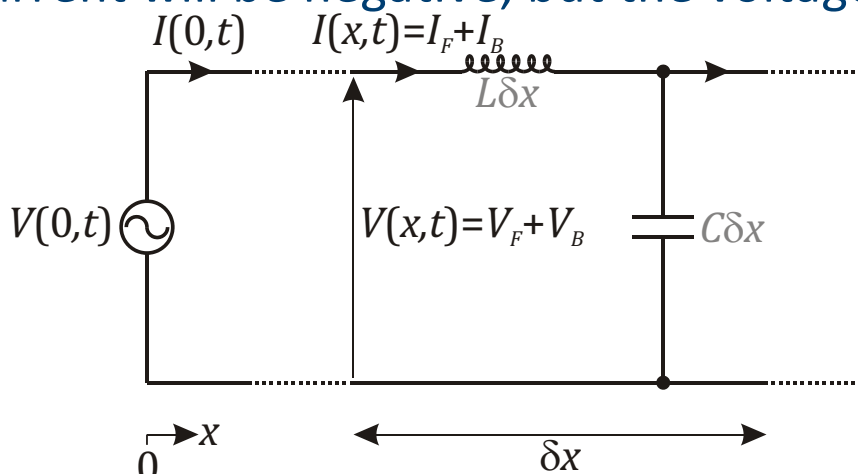

- We can therefore *define* a **Characteristic Impedance**, Z_0 as being *the ratio between the voltage and current of a unidirectional wave at any point on a transmission line*

$$Z_0 = \frac{\overline{V_F}}{\overline{I_F}} = \frac{\overline{V_B}}{-\overline{I_B}} = \frac{\beta}{\omega C} \quad (2.2)$$

- However, $\beta = 2\pi/\lambda$ and $\omega = 2\pi f$, so from Eqn. 1.7


$$\frac{\beta}{\omega} = \frac{1}{c} = \sqrt{LC}$$

- Substituting this into Eqn. 2.2 gives

$$\boxed{Z_0 = \sqrt{L/C}} \quad (2.3)$$

- Z_0 is always a real number for an ideal, lossless line
- Although Z_0 has units of Ω , it **does not dissipate power** as V and I are not between the same point
- It is the apparent impedance that is 'seen' if looking into an infinitely long line at $x = 0$ (i.e. $V(0, t)/I(0, t)$)
- Substitution of L and C for a real transmission line results in an equation of the form
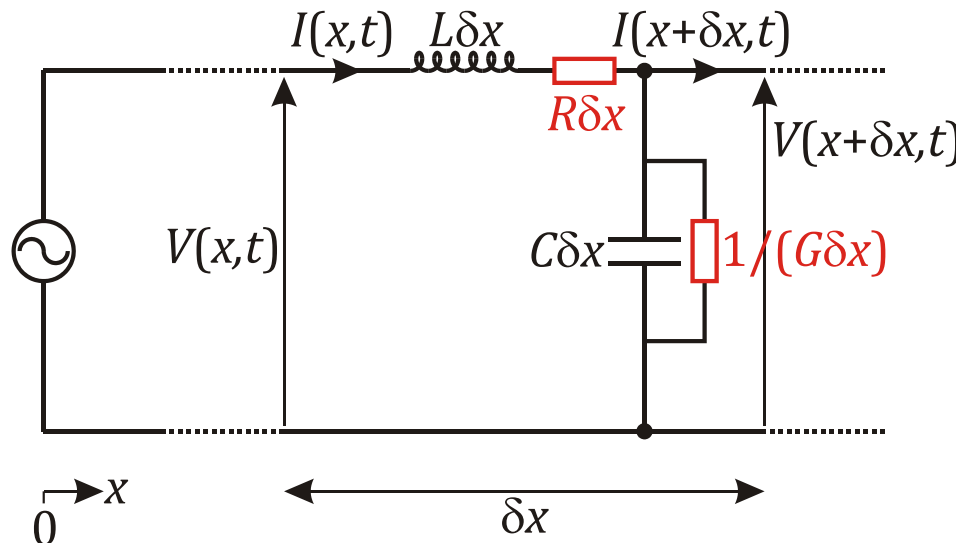
$$Z_0 = \text{Geometry Factor} \times \sqrt{\frac{\mu_0 \mu_r}{\epsilon_0 \epsilon_r}} \quad (2.4)$$



- If the line is 'lossy' then the characteristic impedance gains a frequency dependence


$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (2.5)$$

- Why is the Characteristic Impedance important?
 - Let's imagine that we want to transmit an a.c. signal down a coaxial cable from a signal generator with an output impedance Z_s
 - The maximum power transfer theorem shows that the impedance of a load has to match the output impedance of a source for maximum power transfer into the load
 - Therefore, we need $Z_s = Z_0$ to maximise the signal in the coaxial cable
 - It is for this reason that almost all coaxial cables are either 50Ω or 75Ω and equipment with BNC inputs or outputs are also 50Ω or 75Ω (e.g. the output from a satellite TV receiver box)

Reflections from a Load Impedance

FLE102, GER87

- We will always want to connect our transmission line to something
 - An analogue electronic circuit for processing the signal
 - A digital logic circuit for processing data
 - A load for dissipating power
- Let us consider a situation where we have a wave from some source that is travelling in the forward direction down a transmission line which is terminated in a load impedance Z_L at $x = 0$
- What happens when the wave reaches the load?

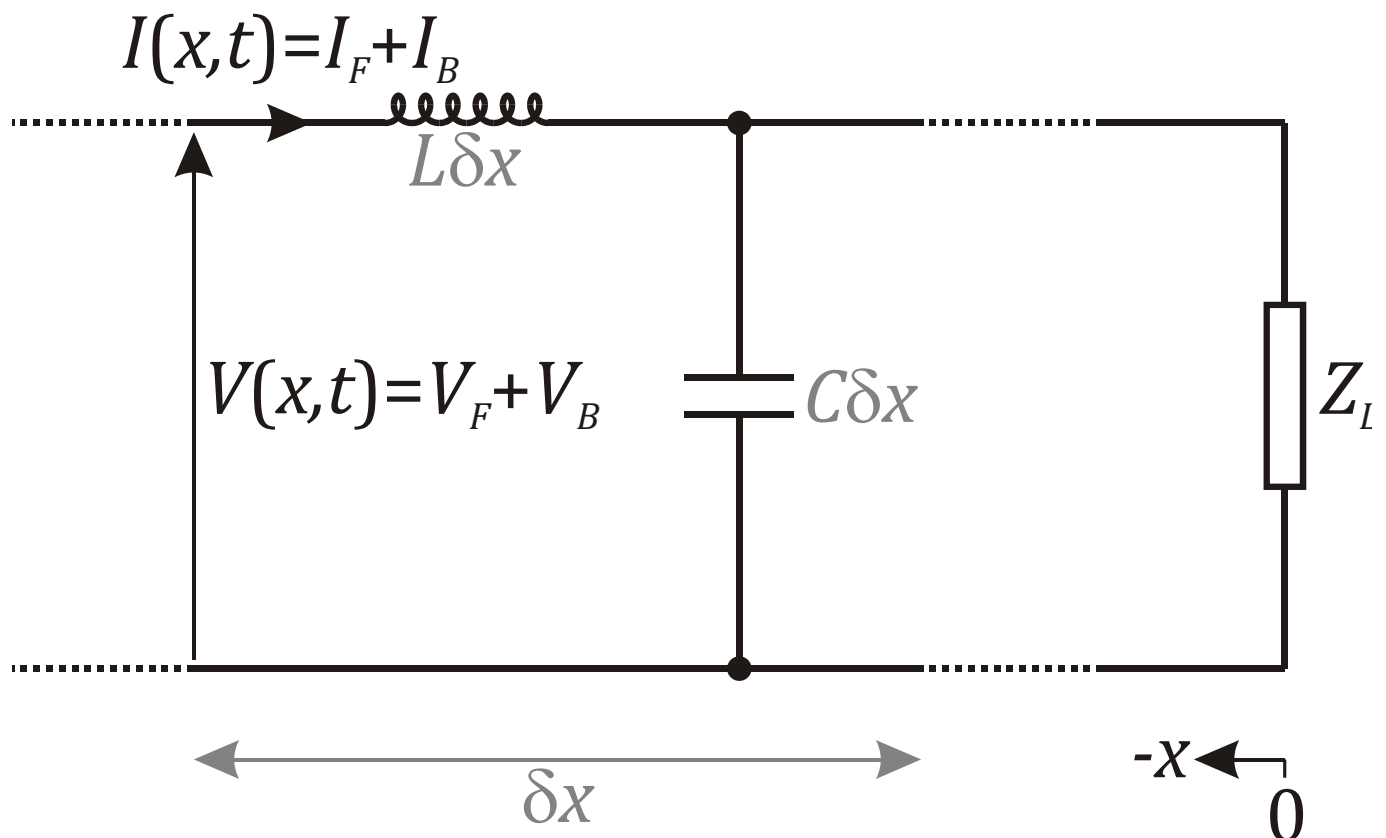

- We clearly have a forward travelling wave from the source, but we should allow for the fact that some of the wave may be reflected by the load to give a backwards travelling wave

- As we have defined the load as being at $x = 0$, Eqns. 1.11 and 1.13 at the load become

$$V(0, t) = \overline{V}_F e^{j(\omega t - \beta 0)} + \overline{V}_B e^{j(\omega t + \beta 0)} = (\overline{V}_F + \overline{V}_B) e^{j\omega t} \quad (2.6)$$

$$I(0, t) = \overline{I}_F e^{j(\omega t - \beta 0)} + \overline{I}_B e^{j(\omega t + \beta 0)} = (\overline{I}_F + \overline{I}_B) e^{j\omega t} \quad (2.7)$$

- As these are the voltage and current across the load Z_L

$$Z_L = \frac{V(0, t)}{I(0, t)} = \frac{(\overline{V}_F + \overline{V}_B)}{(\overline{I}_F + \overline{I}_B)} \quad (2.8)$$

- From Eqn. 2.2 we also know that \overline{V}_F and \overline{I}_F , and \overline{V}_B and \overline{I}_B are related by Z_0 , so we can substitute the currents for voltages

$$Z_L = \frac{(\overline{V}_F + \overline{V}_B)}{(\overline{V}_F/Z_0 - \overline{V}_B/Z_0)} = Z_0 \frac{(\overline{V}_F + \overline{V}_B)}{(\overline{V}_F - \overline{V}_B)} \quad (2.9)$$

- This can be rearranged to make \overline{V}_B the subject so we can see how big the reflected wave is


$$\overline{V}_B = \overline{V}_F \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) \quad (2.9)$$

- We now define the voltage reflection coefficient ρ_L as

5/6 Q6&7


$$\rho_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

(2.10)

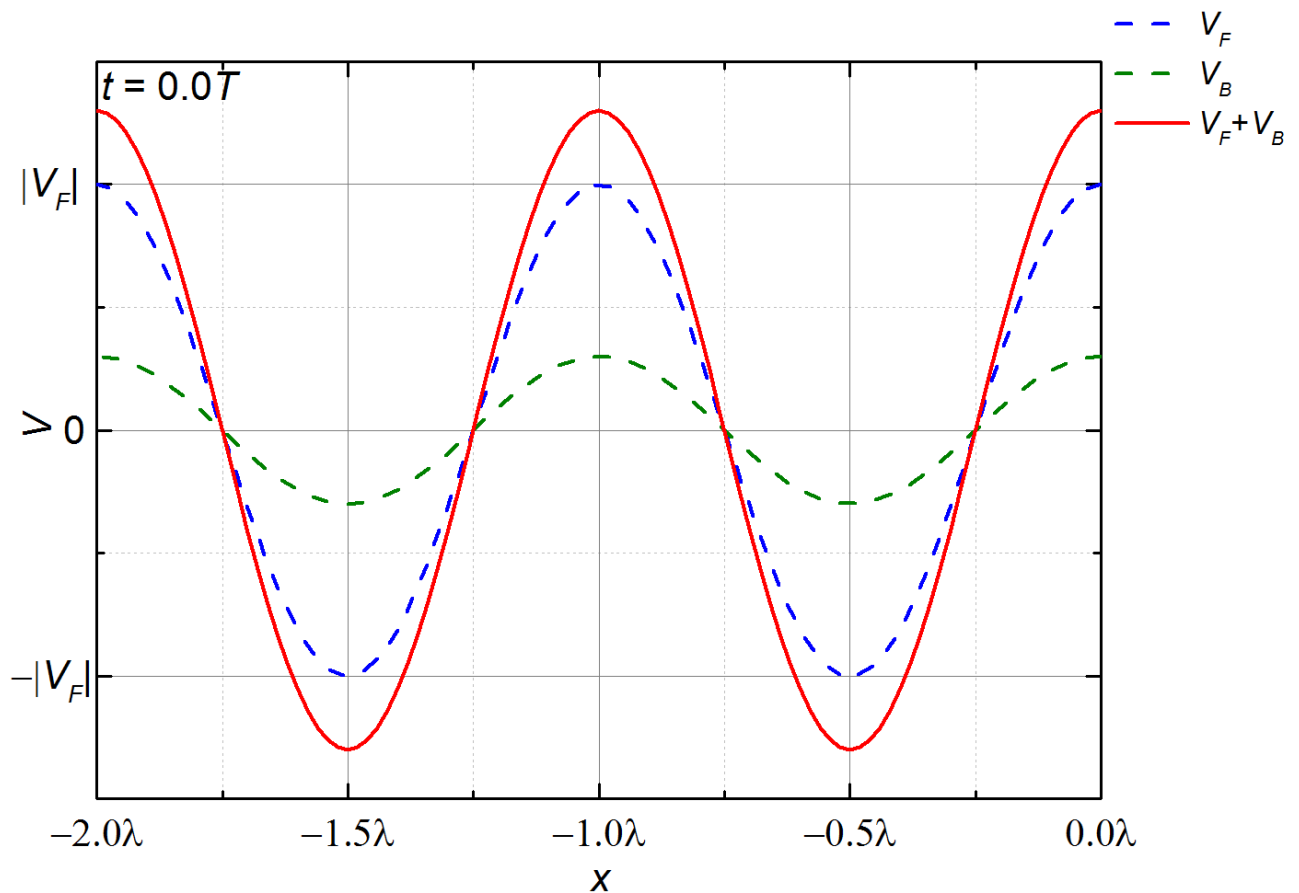

- A proportion ρ_L of the forward wave V_F is being reflected to give a backward wave V_B and these two sum together to produce a **standing wave**

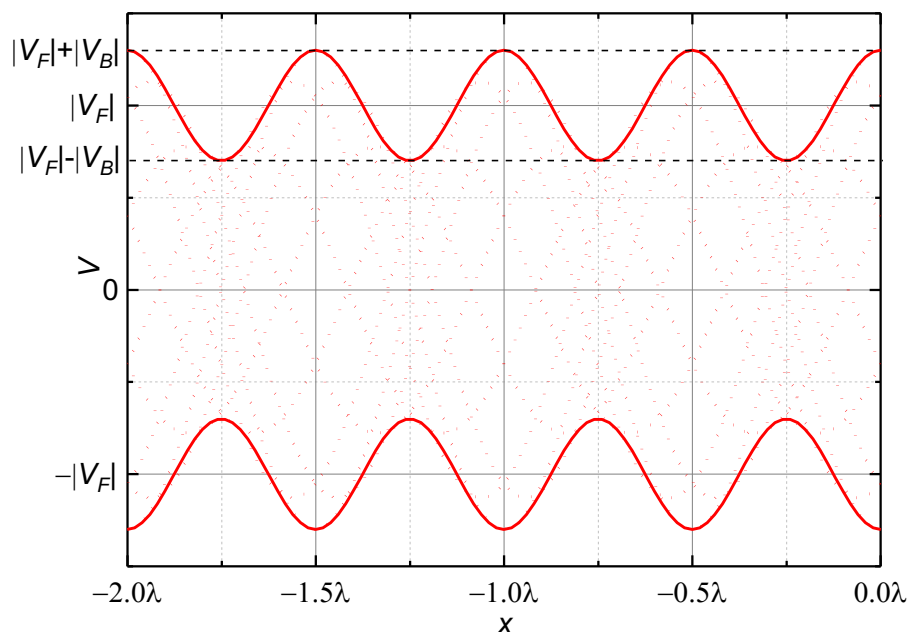
$$V(x, t) = \overline{V_F} (e^{-j\beta x} + \rho_L e^{j\beta x}) e^{j\omega t}$$



- We can define a **voltage standing wave ratio** (VSWR) as being the ratio of the maximum voltage amplitude and minimum voltage amplitude


$$\text{VSWR} = \frac{|\overline{V_F}| + |\overline{V_B}|}{|\overline{V_F}| - |\overline{V_B}|} = \frac{1 + |\rho_L|}{1 - |\rho_L|} \quad (2.11)$$

- If some of the wave is being reflected, then this implies that some power is being reflected too
 - As power is proportional to V^2 then the proportion of the incident power that is reflected is $|\rho_L|^2$
- Three special cases for Z_L now emerge
 - If the transmission line is terminated with an **open circuit**, then $Z_L = \infty$ and $\rho_L = 1$
 - The incident wave is reflected with no change in phase for voltage at the reflection point
 - A perfect standing wave ($\text{VSWR} = \infty$) is formed with an antinode at the reflection point

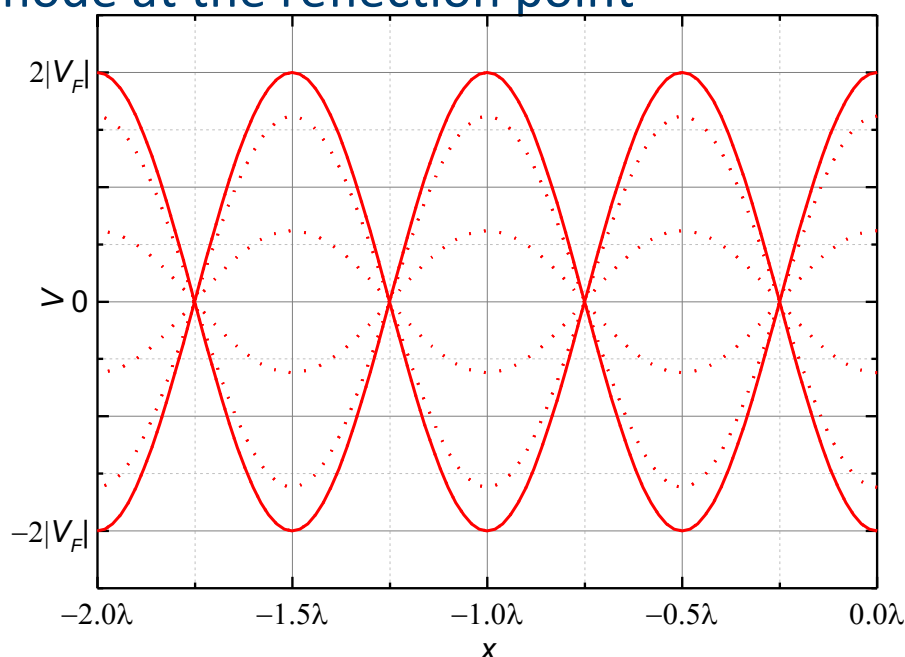

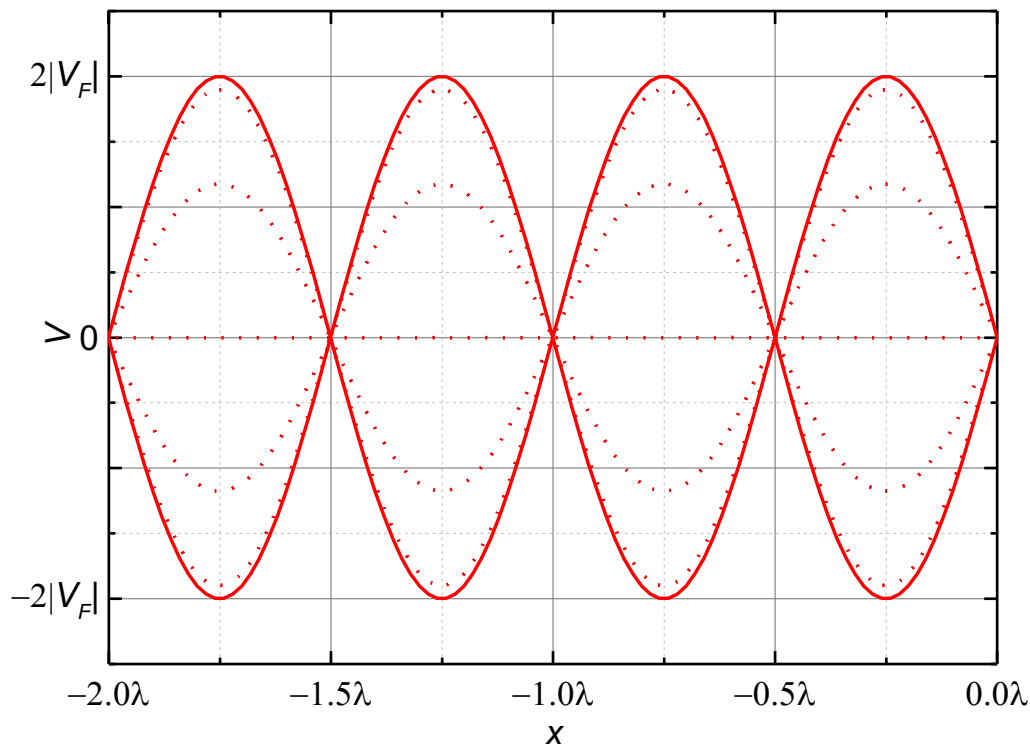2. If the transmission line is terminated with a **closed circuit**, then $Z_L = 0$ and $\rho_L = -1$

- The incident wave is reflected with a π phase change for voltage at the reflection point
- A perfect standing wave ($VSWR = \infty$) is formed with a node at the reflection point




3. If the transmission line is terminated with a load whose impedance is the same as the characteristic impedance of the transmission line ($Z_L = Z_0$) then $\rho_L = 0$

- No wave is reflected and all of the power is dissipated in the load
- This is the ideal scenario for most situations, such as the BNC signal input to a television, which is made to present a load of $50\ \Omega$ to match the characteristic impedance of the coaxial cable supplying the signal

Input Impedance of a Terminated Line

FLE109

- Very often, we have to connect our line to a load that is not a matched impedance
 - An example might be a WiFi box where we are trying to broadcast a 2.45 GHz signal from an antenna
 - The antenna is designed to maximise the broadcast power, and so its impedance might not be equal to the cable supplying the signal
 - We will want to attach a signal source to the input of the cable, and so we will need to know what impedance the source will 'see'
- Let us take a scenario where the cable has a characteristic impedance Z_0
 - It is terminated with an impedance of Z_L at $x = 0$
 - The cable has a length l , and so the input is at $x = -l$

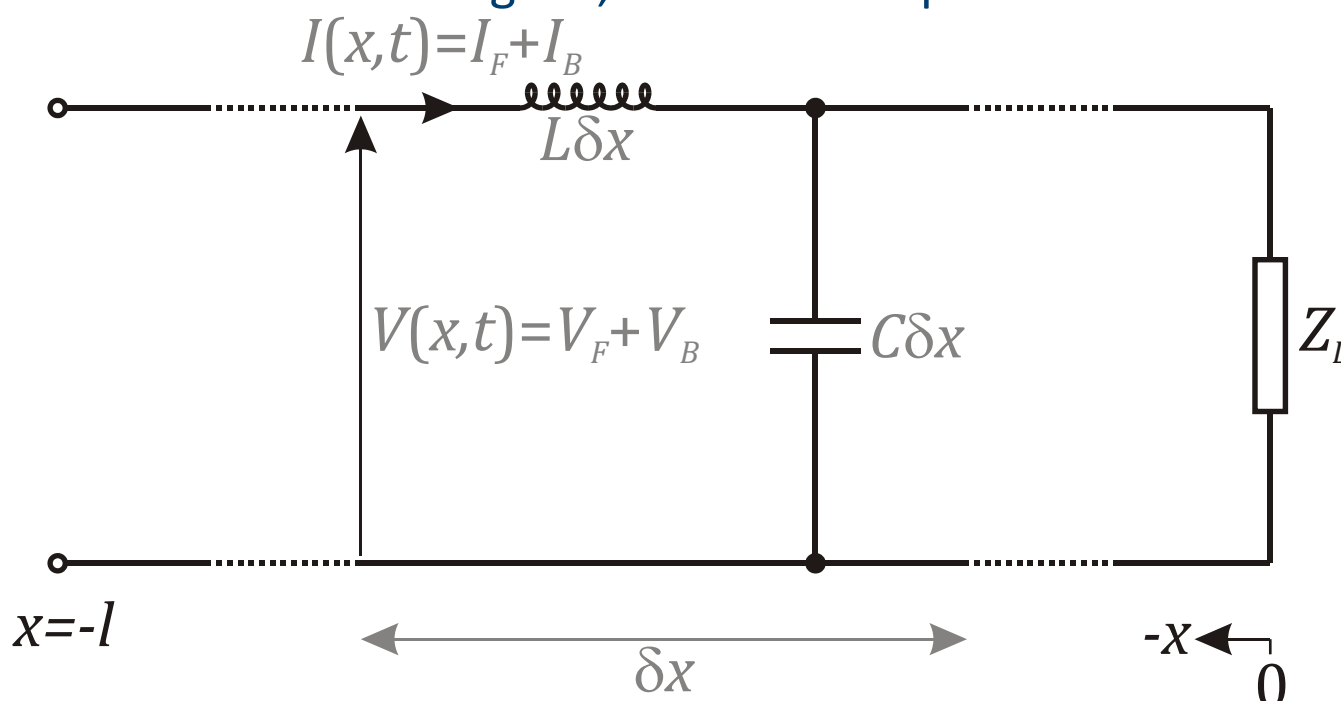

- We can calculate an apparent impedance at any point x in the line as being simply the ratio of the voltage to current at that point using Eqns. 1.11 and 1.13

$$Z(x) = \frac{\overline{V}_F e^{j(\omega t - \beta x)} + \overline{V}_B e^{j(\omega t + \beta x)}}{\overline{I}_F e^{j(\omega t - \beta x)} + \overline{I}_B e^{j(\omega t + \beta x)}} \quad (2.12)$$

- We can lose a factor of $e^{j\omega t}$ and use the characteristic impedance to turn currents into voltages (Eqn. 2.2)

$$Z(x) = \frac{\overline{V}_F e^{-j\beta x} + \overline{V}_B e^{j\beta x}}{\frac{\overline{V}_F}{Z_0} e^{-j\beta x} - \frac{\overline{V}_B}{Z_0} e^{j\beta x}} \quad (2.13)$$

- We can also divide all through by \overline{V}_F

$$Z(x) = Z_0 \frac{e^{-j\beta x} + \frac{\overline{V}_B}{\overline{V}_F} e^{j\beta x}}{e^{-j\beta x} - \frac{\overline{V}_B}{\overline{V}_F} e^{j\beta x}} \quad (2.14)$$

- This allows us to re-express the apparent impedance in terms of the voltage reflection coefficient using Eqn. 2.9

$$Z(x) = Z_0 \frac{e^{-j\beta x} + \rho_L e^{j\beta x}}{e^{-j\beta x} - \rho_L e^{j\beta x}} \quad (2.15)$$

- We can also explicitly show the dependence on Z_L using Eqn. 2.10

$$Z(x) = Z_0 \frac{(Z_L + Z_0)e^{-j\beta x} + (Z_L - Z_0)e^{j\beta x}}{(Z_L + Z_0)e^{-j\beta x} - (Z_L - Z_0)e^{j\beta x}} \quad (2.16)$$


- In this situation, it turns out to be easier to visualise what is going on if we use the de Moivre Theorem to turn our complex exponentials into trigonometric functions

$$Z(x) = Z_0 \frac{Z_L \cos(\beta x) - jZ_0 \sin(\beta x)}{-jZ_L \sin(\beta x) + Z_0 \cos(\beta x)} \quad (2.16)$$

- Therefore, the impedance looking into the line of length l is

$$Z(x = -l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \quad (2.17)$$

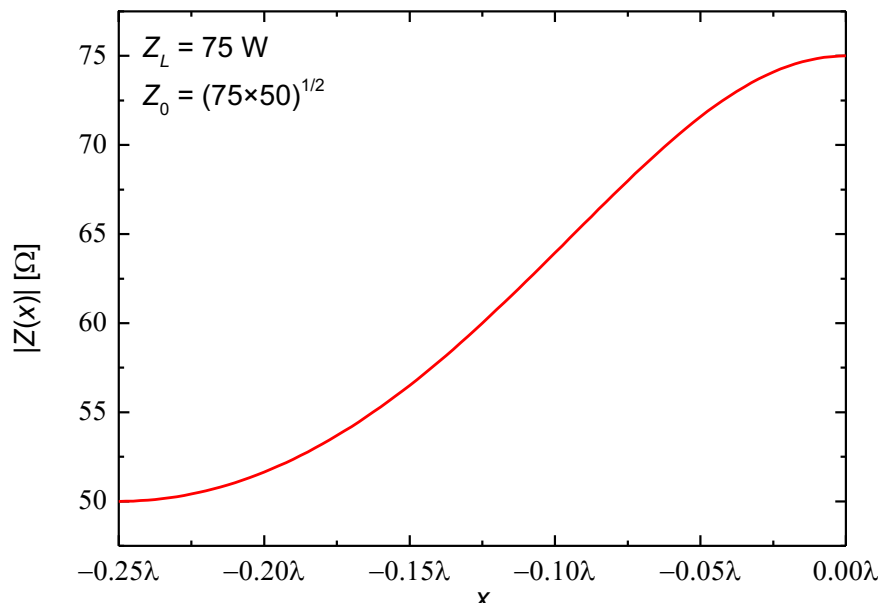- The input impedance depends on the length of the line



- In particular, there is an interesting effect when the length of the line $l = \lambda/4$, as at this point $\beta l = \pi/2$ and $\tan(\beta l) = \infty$

$$Z(x = -\lambda/4) = Z_0 \frac{Z_L + jZ_0 \infty}{Z_0 + jZ_L \infty}$$

$$Z(x = -\lambda/4) = \frac{Z_0^2}{Z_L} \quad (2.18)$$

- We can use this phenomenon to connect mismatched loads to a transmission line

5/6 Q8

- The technique is called ***quarter wave matching***
- For example, imagine that we wish to connect a transmission line with a characteristic impedance of $50\ \Omega$ to a load impedance of $75\ \Omega$ without any reflections
- We connect a short length of another transmission line between the $50\ \Omega$ line and the load
- This additional line should have a length of $\lambda/4$ and a characteristic impedance, Z_0 , equal to the geometric mean of the $50\ \Omega$ transmission line and the load, so

$$Z_0 = \sqrt{Z_L Z_{in}}$$



- This 'matching line' will appear to have an input impedance of $50\ \Omega$, and so it will not cause any reflections at the junction with the $50\ \Omega$ transmission line as their impedances are the same
- The apparent impedance then appears to vary smoothly up to $75\ \Omega$ at the load
- As the load is also $75\ \Omega$, then there is no reflection here either
- All the input power is therefore dissipated in the load with no reflections, as required

Ringing


FLE112

- A common scenario is that we wish to send a digital data signal down a transmission line
 - Ideally this should be a square wave, but in practice it takes some time for the voltage to settle after each change

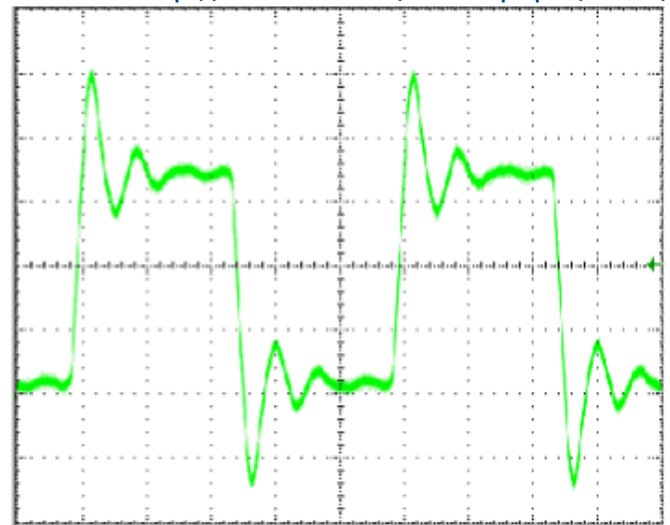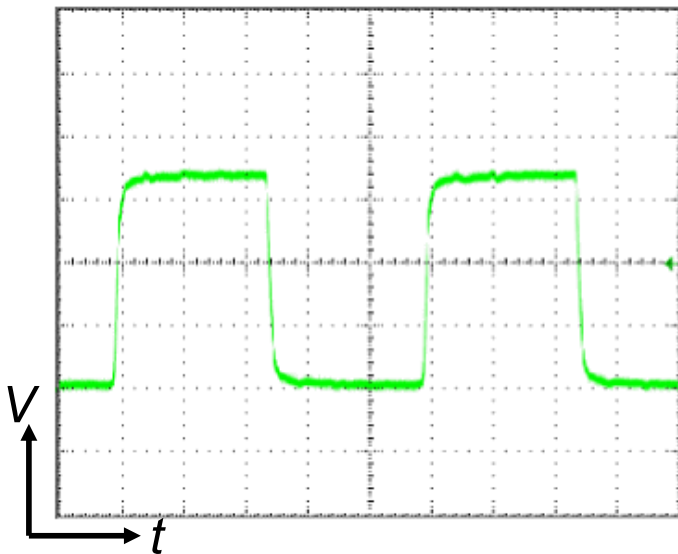From <http://www.ni.com/white-paper/3854/en/>



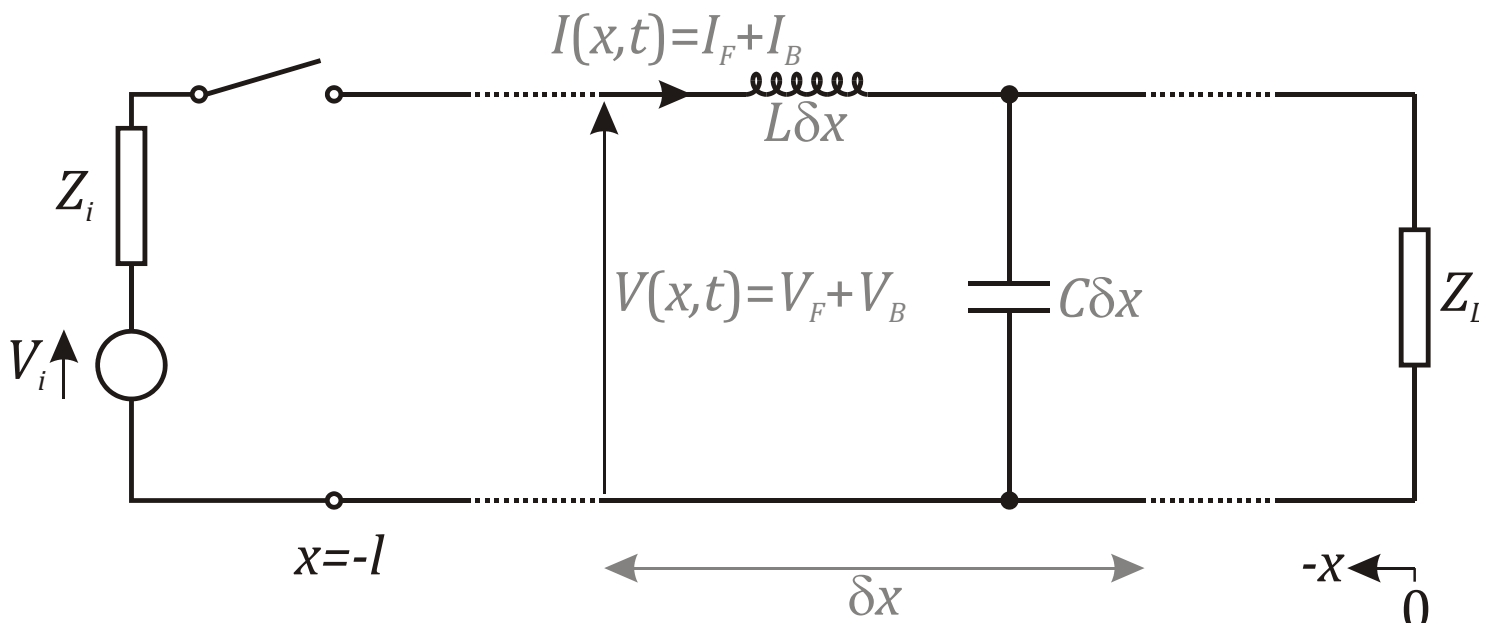- Let us consider applying our input signal using a simple voltage source with an impedance Z_i and a switch connected to the transmission line of length l



- Let the switch close at time $t = 0$
- At that moment, the load impedance can have no effect on the input to the line, so, treating this as a simple potential divider, the voltage transmitted into the line is

$$V(x = -l, t = 0) = V_i \left(\frac{Z_0}{Z_i + Z_0} \right)$$

- This voltage will then be transmitted along the line at the wave velocity $c = 1/\sqrt{LC}$ (from Eqn. 1.7), arriving at the load some time T later, where

$$T = l/c = l\sqrt{LC}$$

- Upon reaching the load, the reflection coefficient will determine how much of the wave is reflected (Eqn. 2.10),

$$\rho_L = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right)$$

- This will sum with the input voltage to give

$$V(x = 0, t = T) = V_i \left(\frac{Z_0}{Z_i + Z_0} \right) [1 + \rho_L] \quad (2.19)$$

- This will then take a further time T to travel back to the input end of the transmission line, where the reflected component will itself be reflected again with Z_i now looking like the load, so

$$\rho_i = \left(\frac{Z_i - Z_0}{Z_i + Z_0} \right)$$

- Hence

$$V(x = -l, t = 2T) = V_i \left(\frac{Z_0}{Z_i + Z_0} \right) [1 + \rho_L + \rho_L \rho_i] \quad (2.20)$$


- If there is another complete round-trip of reflections, then the voltage at the input will be

$$\begin{aligned} V(x = -l, t = 4T) \\ = V_i \left(\frac{Z_0}{Z_i + Z_0} \right) [1 + \rho_L + \rho_L \rho_i + \rho_L^2 \rho_i + \rho_L^2 \rho_i^2] \end{aligned} \quad (2.21)$$

- We can now generalise this to a series expression for n round-trips

$$\begin{aligned} V(x = -l, t = 2nT) \\ = V_i \left(\frac{Z_0}{Z_i + Z_0} \right) \left[1 + \sum_{n=1}^n (\rho_L^n \rho_i^{n-1} + \rho_L^n \rho_i^n) \right] \end{aligned} \quad (2.22)$$

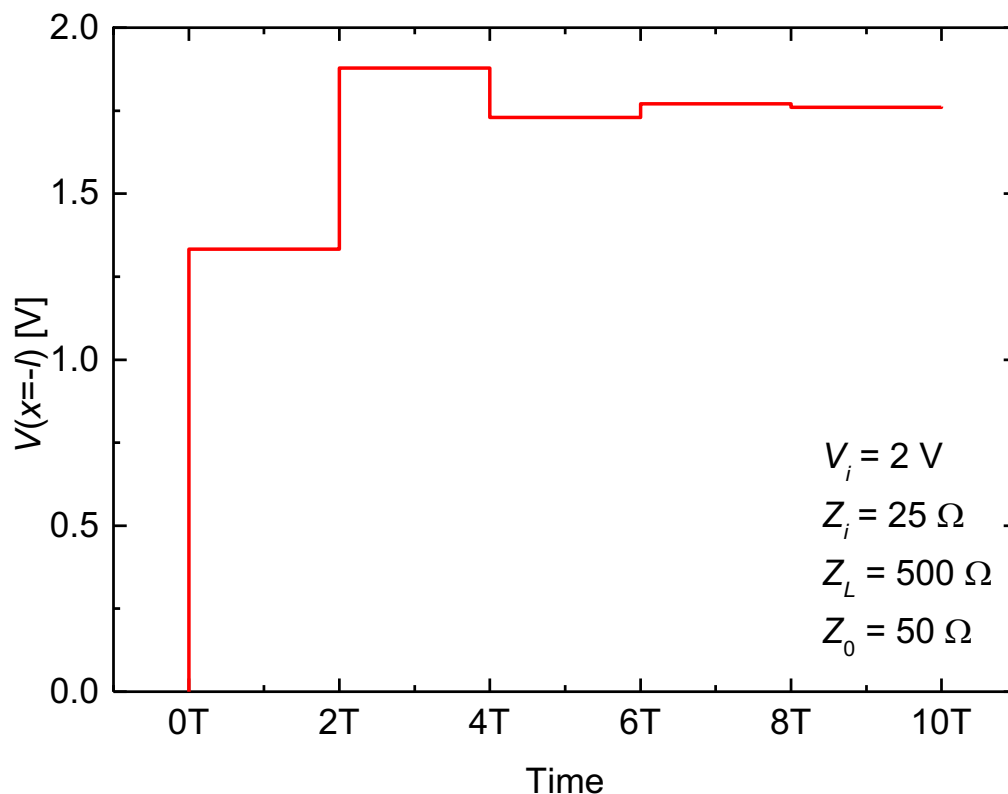- This geometric series then converges with time



5/6 Q9